

Counters:

Counter is a sequential circuit. A digital circuit which is used for a counting pulses is known counter. Counter is the widest application of flip-flops. It is a group of flip-flops with a clock signal applied. Counters are of two types.

- Asynchronous or Ripple Counters
- Synchronous Counters

➤ Classification of Counters:

Depending on the way in which the counting progresses, the synchronous or asynchronous counters are classified as follows –

- Up Counters
- Down Counters
- Up/Down Counters

➤ UP/DOWN Counter:

Up counter and down counter is combined together to obtain an UP/DOWN counter. A mode control (M) input is also provided to select either up or down mode. A combinational circuit is required to be designed and used between each pair of flip-flop in order to achieve the up/down operation.

➤ Type of Up/Down Counters:



There are two types of up/down counters –

- UP/DOWN Ripple Counters
- UP/DOWN Synchronous Counter


➤ UP/DOWN Ripple Counters:

In the UP/DOWN ripple counter all the FFs operate in the toggle mode. So either T flip-flops or JK flip-flops are to be used. The LSB flip-flop receives clock directly. But the clock to every other FF is obtained from ($Q = Q$ bar) output of the previous FF.

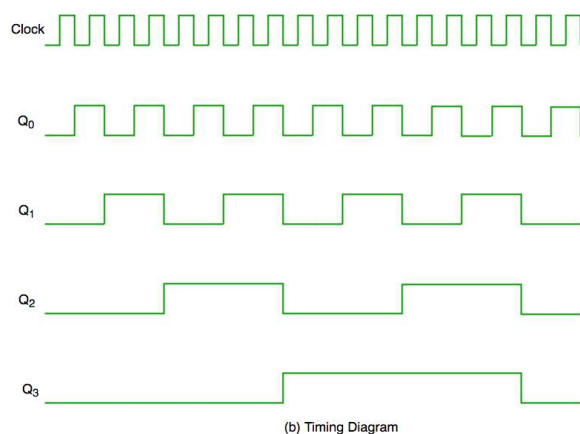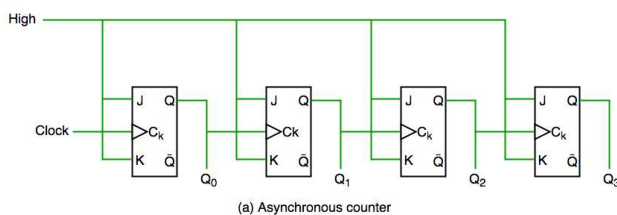- **UP counting mode (M=0)** – The Q output of the preceding FF is connected to the clock of the next stage if up counting is to be achieved. For this mode, the mode select input M is at logic 0 (M=0).
- **DOWN counting mode (M=1)** – If M = 1, then the Q bar output of the preceding FF is connected to the next FF. This will operate the counter in the counting mode.



Asynchronous Counter

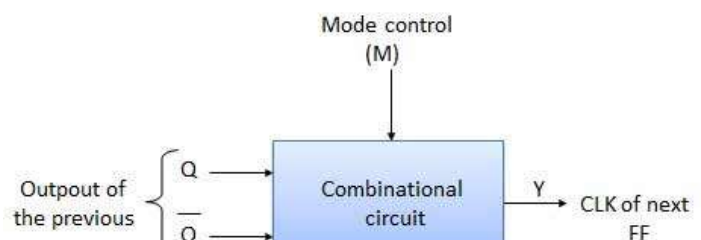

Inputs			Outputs
M	Q	\overline{Q}	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Y = Q
for up
counter

Y = \overline{Q}
for up
counter

Truth Table

